

ETME 4130 Applied Electric Power and Machinery Lab 3: DC Motors

Pre-Lab Analysis:

1. Name five types of DC machines?
2. Which DC machines can supply the highest power to weight ratio?
3. If the DC motor in each of the following cases was initially rotating clockwise. What is the direction of rotation of the motor in each case below:

Case 1: The motor is a series DC motor, and the rotor connection was reversed. _____

Case 2: The motor is a shunt DC motor, and the shunt winding was reversed. _____

Case 3: The motor is a shunt DC motor, and both the rotor winding and the shunt winding connections were reversed. _____

Lab Work:

- Make sure that you wear your safety glasses continuously in the lab
- Make sure that the power is turned off before you start connecting the circuit
- Connect the circuit of each motor shown in the figure. Then reconnect the circuits to reverse the motors. Everytime you finish a connection, raise your hand. Do NOT turn on the power until the professor approves your circuit. A video of the experiment can be found on YouTube at: <https://www.youtube.com/watch?v=GS91ydbwWU>



